

Tutorial o' Answer

- ① Ohm's law states that for a fixed resistor, voltage drop is proportional to current applied - ①
- $$V \propto I$$
- $$V = IR$$
- ①
- 

②

At mesh -1

$$i_1(1+2+4) - i_2(1) - i_3(2) = 230 - 115$$

At mesh -2

$$7i_1 - i_2 - 2i_3 = 115 \quad -①$$

At mesh -3

$$-i_1(1) + i_2(6+3+1) - i_3(3) = 0$$

$$-i_1 + 10i_2 - 3i_3 = 0 \quad -②$$

$$-i_1(3) + i_2(3) + i_3(21+5) = 115 - 460$$

$$-2i_1 - 3i_2 + 10i_3 = -345 \quad -③$$

Solving we get

$$i_1 = 4.4A$$

$$i_2 = -10.6A$$

$$i_3 = -36.8A$$


---

3 marks for 3 mesh equations  
1 mark for result

3 No of nodes = 7 ①

No of mesh = 3 ①

— 2

4 KVL  $\rightarrow$  Kirchhoff's voltage law states that Total voltage drop over any loop is same - ①

Kel  $\rightarrow$  Kirchhoff's current law states that Total current entering a node is equal to Total current leaving a node - ①


on.

KVL  $\sum_{i=1}^n V_i = 0$

Kel  $\sum_{i=1}^n i_k = 0$

— 2

5

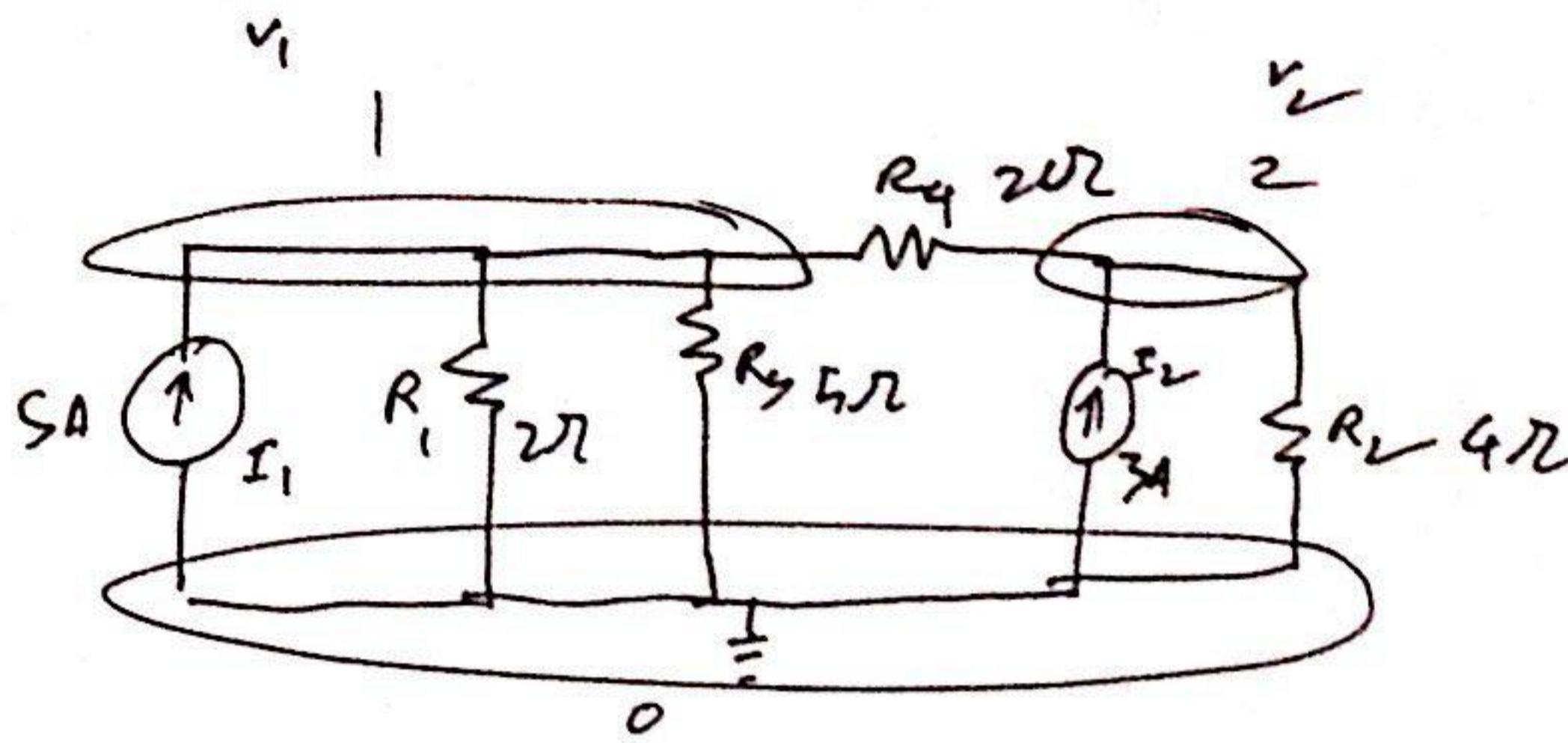

At node -1

$$v_1 \left( \frac{1}{2} + \frac{1}{5} + \frac{1}{2} \right) - v_2 \left( \frac{1}{2} \right) = 5$$

$$1.2v_1 - 0.5v_2 = 5 \quad \text{--- (1)}$$

At node -2

$$-v_1 \left( \frac{1}{2} \right) + v_2 \left( \frac{1}{2} + \frac{1}{4} \right) = 3$$

$$-0.5v_1 + 0.75v_2 = 3 \quad \text{--- (2)}$$

solving 2 equations

$$v_1 = 8.077\text{V}$$

$$v_2 = 9.38\text{V}$$

writing 2 node equation  
solving for  $v_1$  &  $v_2$

$$\begin{array}{rcl} 2xL = 4 \\ -1 \\ \hline 5 \end{array}$$

$$1.2v_1 - 0.5v_2 = 5 \quad \text{--- (1)}$$

$$-0.5v_1 + 0.75v_2 = 3 \quad \text{--- (2)}$$

$$\begin{array}{rcl} (1) \times 1.5 & 1.8v_1 - 0.75v_2 = 7.5 \\ (+1) \frac{1.3v_1}{v_1} & = 10.5 \\ & v_1 = 8.077\text{V} \end{array}$$

$$\begin{aligned} v_2 &= 2(1.2v_1 - 5) \\ &= 9.38\text{V} \end{aligned}$$