

**CSE 100: Computer Skills**

**Lecture 7: Digital Systems  
-Boolean Algebra**

Shahadat Hussain Parvez

**Boolean Algebra**

- A Boolean variable is that has only 2 possible values
  - TRUE or FALSE
  - HIGH or LOW
- Boolean variables are logical variables
- Algebra with these Boolean variables is called Boolean Algebra
- Operator that operate on Boolean variables are called Boolean operator or logical operator

3/9/2018 SHP

2


**Logic operation and gates**

- Logical operations are implemented by various electronic circuits
- These circuits are called logic gates
- Fundamental Gates include
  - OR gate
  - AND gate
  - NOT gate
- Other gates include
  - NOR gate
  - NAND gate
  - XOR gate
  - XNOR gate


3/9/2018 SHP

3

**OR operation**

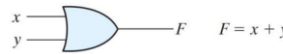


x	y	F
0	0	0
0	1	1
1	0	1
1	1	1

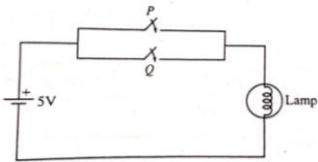


3/9/2018 SHP

4

**AND operation**




x	y	F
0	0	0
0	1	0
1	0	0
1	1	1

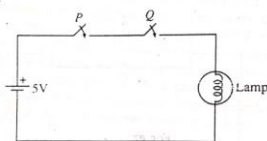

3/9/2018 SHP


5

**NOT operation**



x	F
0	1
1	0

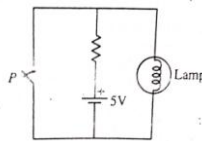Note that the NOT or complement can be written both as  $X'$  and  $\bar{X}$



3/9/2018 SHP

6

## Functional Gates


- Some simple Boolean functions are often expressed as single operation
- Different gate is used to implement that
- Common functional gates are
  - NOR gate
  - NAND gate
  - XOR gate
  - XNOR gate

3/9/2018 SHP

7
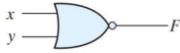
## NOR Gate

- Basically a OR gate followed by a NOT gate



$F = (x + y)'$


x	y	F
0	0	1
0	1	0
1	0	0
1	1	0

3/9/2018 SHP

8
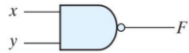
## NAND Gate

- Basically an AND gate followed by a NOT Gate



$F = (xy)'$


x	y	F
0	0	1
0	1	1
1	0	1
1	1	0

3/9/2018 SHP

9

## XOR Gate

- Also known as exclusive OR



$F = xy' + x'y$   
 $= x \oplus y$


x	y	F
0	0	0
0	1	1
1	0	1
1	1	0

3/9/2018 SHP

10
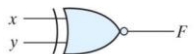
## XNOR Gate

- Basically an XOR gate followed by a NOT gate



$F = xy + x'y'$   
 $= (x \oplus y)'$

x	y	F
0	0	1
0	1	0
1	0	0
1	1	1

3/9/2018 SHP

11


## Universal Gates

- NOR and NAND gates called universal gate
- They can simulate any fundamental gates
- Therefore can implement any logic functions

3/9/2018 SHP


12

### Fundamental gates using NOR

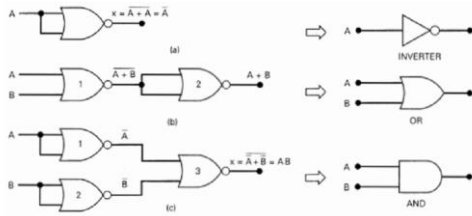

3/9/2018 SHP 13

### Fundamental gates using NAND

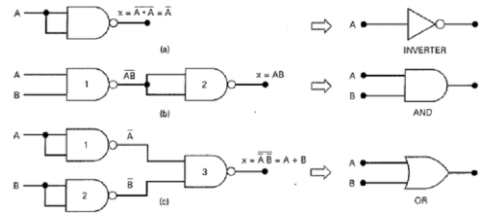

3/9/2018 SHP 14

### Boolean Functions and Truth Table

- The OR and AND operators can be applied on more than two operands
- Combining the operators and operands Boolean expression are formed
- The Order of precedence is NOT,AND, and then OR
- A truth table is simply the tabular representation of Boolean function

3/9/2018 SHP 15

### Truth table from Boolean Functions

- Steps are as follows
  1. Count in binary with each number having as many bits as the number of variables. Put each number in a row in the table
  2. Now for each row calculate the value of the function

3/9/2018 SHP 16

### Finding Function from truth table

- Sum of minterms are used to make functions

Minterms			
x	y	z	Term Designation
0	0	0	$x'y'z'$ $m_0$
0	0	1	$x'y'z$ $m_1$
0	1	0	$x'yz'$ $m_2$
0	1	1	$x'yz$ $m_3$
1	0	0	$xy'z'$ $m_4$
1	0	1	$xy'z$ $m_5$
1	1	0	$xyz'$ $m_6$
1	1	1	$xyz$ $m_7$

3/9/2018 SHP 17

### Finding Function from truth table

X	Y	W	Z	Minterms
0	0	0	0	$\bar{X}\bar{Y}\bar{W}$
0	0	1	1	$\bar{X}\bar{Y}W$ ✓
0	1	0	0	$\bar{X}Y\bar{W}$
0	1	1	0	$\bar{X}YW$
1	0	0	1	$X\bar{Y}\bar{W}$ ✓
1	0	1	1	$X\bar{Y}W$ ✓
1	1	0	1	$XY\bar{W}$ ✓
1	1	1	1	$XYW$ ✓

The function is  $Z = X'Y'W + XY'W' + XY'W + XYW' + XYW$

3/9/2018 SHP 18

## Boolean Postulates and Laws

Boolean algebra follows some postulates. For any boolean variable  $X$ , the postulates are the following.

- (1)  $X + 0 = X, X \cdot 1 = X$  (2)  $X + X = X, X \cdot X = X$   
 (3)  $X + 1 = 1, X \cdot 0 = 0$  (4)  $X + \bar{X} = 1, X \cdot \bar{X} = 0$   
 (5)  $\bar{\bar{X}} = X$

Apart from these postulates, boolean algebra also follows the commutative, associative and distributive laws like ordinary algebra. For any boolean variables  $W, X, Y$  and  $Z$  these law mean the following.

Commutative Law  $X + Y = Y + X$   
 $X \cdot Y = Y \cdot X$   
 Associative Law  $X + (Y + Z) = (X + Y) + Z = X + Y + Z$   
 $X \cdot (Y \cdot Z) = (X \cdot Y) \cdot Z = X \cdot Y \cdot Z$   
 Distributive Law  $X(Y + Z) = XY + XZ$   
 $(W + X)(Y + Z) = WY + WZ + XY + XZ$

These postulates and laws are used to simplify boolean functions.

3/9/2018 SHP

19

## De Morgan's Theorem

Augustus De Morgan has given two useful theorems for boolean algebra. They are the following.

- **First Theorem:** For any two boolean variables  $X$  and  $Y$ ,  $\overline{X+Y} = \bar{X}\bar{Y}$ .
- **Second Theorem:** For any two boolean variables  $X$  and  $Y$ ,  $\overline{X \cdot Y} = \bar{X} + \bar{Y}$ .

These theorems are also true for any number of variables. Using truth table, they can be proved easily.

3/9/2018 SHP

20

## Simplification of Functions

- Simplification of Boolean Logic allows for implementation with fewer number of gates
- Similar to normal Algebra
- Steps of simplification are as follows
  - Terms with Parenthesis are evaluated first
  - The Order of precedence is NOT, AND, and then OR
  - In every step Boolean Postulates, laws and theorem are used where necessary

3/9/2018 SHP

21

## Simplification of Functions

**Example 2.44:** Simplify  $F = \bar{X}(X + Y)$ .  
**Solution:**

$$\begin{aligned} F &= \bar{X}(X + Y) \\ &= \bar{X}X + \bar{X}Y \quad [\text{Using distributive law.}] \\ &= 0 + \bar{X}Y \quad [\text{Using postulate } \bar{X}X = 0.] \\ &= \bar{X}Y \quad [\text{Using postulate } X + 0 = X.] \end{aligned}$$

**Example 2.45:** Simplify  $\overline{(A + B + C)}\bar{B}$ .  
**Solution:**

$$\begin{aligned} \overline{(A + B + C)}\bar{B} &= (\bar{A}\bar{B}\bar{C})\bar{B} \quad [\text{Using De Morgan's law.}] \\ &= (\bar{A}\bar{B}\bar{C})\bar{B} \quad [\text{Using the postulate } \bar{X}\bar{X} = \bar{X}.] \\ &= \bar{A}\bar{B}\bar{B}\bar{C} \quad [\text{Using commutative law.}] \\ &= \bar{A}\bar{B}\bar{C} \quad [\text{Using the postulate } X \cdot X = X.] \end{aligned}$$

3/9/2018 SHP

22

## Simplification of Functions

**Example 2.46:** Simplify  $F = A\bar{B} + \bar{A}\bar{B} + AB$ .  
**Solution:**

$$\begin{aligned} F &= A\bar{B} + \bar{A}\bar{B} + AB \\ &= (A + \bar{A})\bar{B} + AB \\ &= (1)\bar{B} + AB \quad [\text{Using postulate } \bar{X} + X = 1.] \\ &= \bar{B} + AB \end{aligned}$$

3/9/2018 SHP

23

## LOGIC CIRCUIT

3/9/2018 SHP

24

### Logic Circuit from Logic Functions

**Example 2.47:** Implement the XOR function using basic gates.  
**Solution:** From the truth table of XOR it is obvious that the output  $X = P\bar{Q} + P\bar{Q}$ . Hence implementation of  $X = P\bar{Q} + P\bar{Q}$  is shown in Figure 2.15.

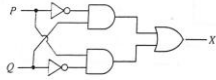


Figure 2.15: XOR function using basic gates.

### Logic Circuit from Logic Functions

**Example 2.48:** Implement  $X = AF + A(C + D)$  using logic gates.  
**Solution:** The implementation is shown in Figure 2.19.

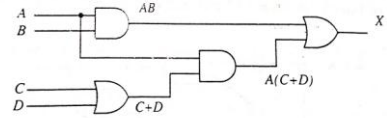


Figure 2.19: Implementation of  $X = AB + A(C + D)$ .

### Logic Circuit from Logic Functions

**Example 2.49:** Draw a logic circuit for  $X = \overline{(AB + C)} \cdot (AC \oplus \bar{B})$ .  
**Solution:** The circuit is drawn in Figure 2.20.

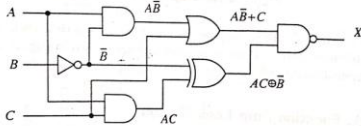


Figure 2.20: Implementation of  $X = \overline{(AB + C)} \cdot (AC \oplus \bar{B})$ .

### Logic Circuit from Logic Functions

**Example 2.50:** Draw implementation of  $X = [D + (\bar{A+B}) \cdot \bar{C}] \cdot E$  using logic gates.  
**Solution:** The implementation is drawn in Figure 2.21.

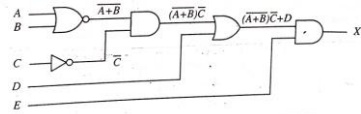


Figure 2.21: Implementation of  $X = [D + (\bar{A+B}) \cdot \bar{C}] \cdot E$ .

### Logic Circuit from Logic Functions

**Example 2.51:** Implement a circuit to add two binary bits.  
**Solution:** As we know, if two binary bits  $A$  and  $B$  are added there will be a sum ( $S$ ) and a carry ( $C$ ). For different values of  $A$  and  $B$ , values of  $S$  and  $C$  can be copied from the rules of binary addition and put into a truth table. The truth table is shown in Table 2.7.

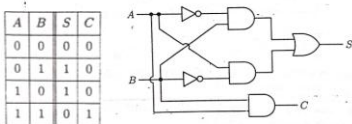


Figure 2.22: Single bit binary adder.

### Logic Function from Logic circuit


• The steps involved are

1. Label the inputs of all the first level gates
2. Compute their outputs
3. Propagate these outputs to inputs of other gates of next level
4. Repeat until last level output is found

## Logic Function from Logic circuit

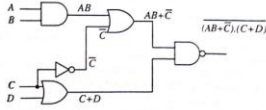**Example 2.52:** Derive the boolean function of the logic circuit of Figure 2.23.

**Solution:** As the inputs of gates on the left (level 1) are already labeled we proceed to find the outputs of these gates. The upper AND gate will output  $AB$ , the NOT will output  $\bar{C}$  and the lower OR gate's output will be  $C + D$ . This is shown in Figure 2.24. Now propagate these to the inputs of OR and NAND gates on the right. The OR gate on top, will have  $AB$  and  $\bar{C}$  on its inputs and so will produce  $AB + \bar{C}$  on output. This will feed the last NAND gate. The other input of the NAND will come from the output of lower OR gate. This is  $C + D$ . If  $AB + \bar{C} = X$  and  $C + D = Y$  are the inputs of the NAND, its output will be  $\overline{XY}$  which evaluates to  $\overline{(AB + \bar{C})(C + D)}$ .



3/9/2018 SHP

31

## Homework Based on Lecture 7

- Questions from Chapter 2, Introduction to computers by Mohammed Alamgir
- Example 2.40-2.52
- Exercise 37, 38, 40, 41, 42, 43, 44, 47, 48, 49, 50, 51, 52, 53, 56, 58,

3/9/2018 SHP

32

END

3/9/2018 SHP

33