

# CSE 122 LAB 4

North East University Bangladesh

Department of CSE

Course no: CSE 122

Experiment no: 04

Experiment Name: Verification of Superposition and Thevenin Theorem

## CAUTIONS:

1. Don't switch on the supply of the circuit until you have verified the circuit carefully
2. Take readings of apparatus carefully
3. Take care of any bare circuit elements in energized condition
4. Never try to touch bare live wires

## Part A: Verification of Superposition Principle

### Objective

To verify experimentally the Superposition theorem this is an analytical technique of determining currents in a circuit with more than one emf source.

### Theory

In a linear circuit containing multiple independent sources and linear elements (e.g. resistors, inductors, capacitors) the voltage across (or the current through) any element when all the sources are acting simultaneously may be obtained by adding algebraically all the individual voltages ( or the currents ) caused by each independent source acting alone, with all other sources deactivated.


An independent voltage source is deactivated (made zero) by shorting it and an independent current source is deactivated (made zero) by open circuiting it. However, if a dependent source is present it must remain active during the superposition process.

### Apparatus Needed

- Trainer Board (Bread board)
- DC Voltmeter
- DC Ammeter
- Three Rheostats
- One multimeter
- Connecting wires

### Procedure

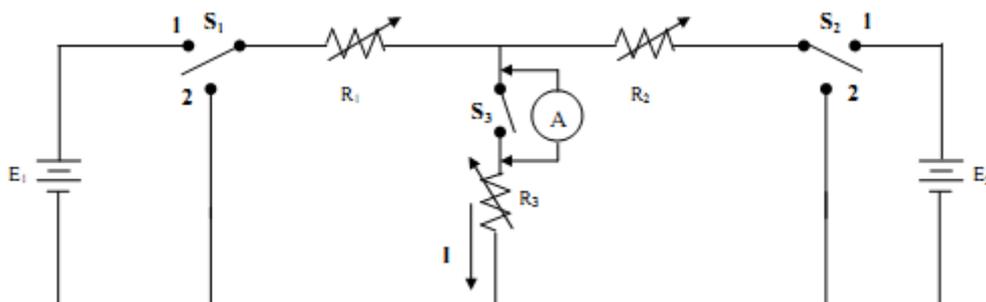1. Set up the circuit as in the figure below



2. Keep both sources active by keeping  $S_1$  &  $S_2$  in the proper position (position 1).
3. Apply 5 volts from  $E_1$  and 7 volts from  $E_2$ .
4. Set the rheostats  $R_1$ ,  $R_2$  &  $R_3$  above  $20\Omega$ . [Alternatively use fixed resistors above  $20\Omega$ ]

## CSE 122 LAB 4

5. Measure the current  $I$  and record it in the given table.
6. Render  $E_2$  inactive (keeping  $E_1$  active) & measure the current  $I'$  in the branch  $R_2$ .
7. Render  $E_1$  inactive (keeping  $E_2$  active) & Measure the current  $I''$  in the branch  $R_2$ .
8. Verify if  $I = I' + I''$  which would validate the superposition theorem for this particular circuit.
9. Repeat steps 4 to 7 by changing  $R_1, R_2, R_3$  and take a few more sets of readings.

**Table**

No. of Obs.	$R_1$ (ohms)	$R_2$ (ohms)	$R_3$ (ohms)	$I_2$ with both $E_1$ and $E_2$ active (amps)	$I_2'$ with only $E_1$ active (amps)	$I_2''$ with only $E_2$ active (amps)
1.						
2.						
3.						

**Result**

1. Show the results in tabular form
2. Comment on the obtained results and discrepancies

### Part B: Verification of Thevenin's Theorem

**Objective**

To verify Thevenin's theorem with reference to a given circuit theoretically as well as experimentally.


**Theory**

It is often desirable in circuit analysis to study the effect of changing a particular branch element while all other branches and all the sources in the circuit remain unchanged. Thevenin's theorem is a technique to this end and it reduces greatly the amount of computations which we have to do each time a change is made. Using Thevenin's theorem the given circuit excepting the particular branch to be studied is reduced to the simplest equivalent circuit possible and then the branch to be changed is connected across the equivalent circuit.

The Thevenin's theorem states that any two terminal linear bilateral network containing sources and passive elements can be replaced by an equivalent circuit consist of a voltage source  $V_{th}$  in series a resistor  $R_{th}$  where

$V_{th}$  = The open circuit voltage ( $V_{OC}$ ) at the two terminals A & B.

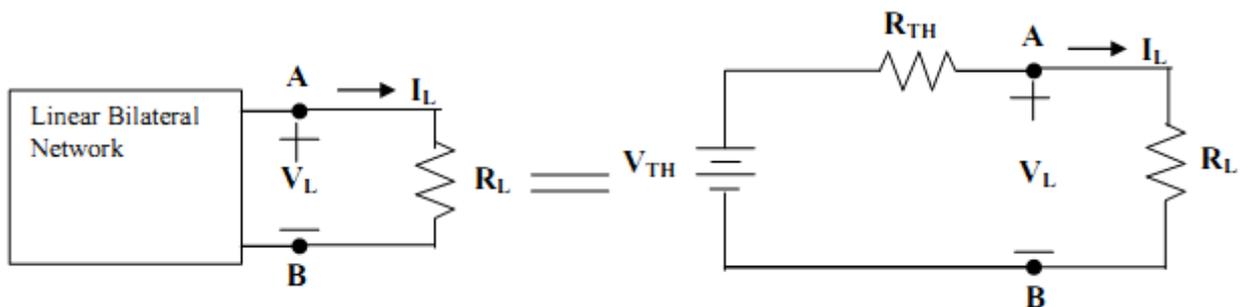
$R_{th}$  = The resistance looking into the terminals A and B of the network with all sources removed.



There are several methods for determining Thevenin resistance  $R_{TH}$ . An attractive method for determining  $R_{TH}$  is: (1) determine the open circuit voltage, and (2) determine the short circuit current  $I_{SC}$  as shown in the figure; then

## CSE 122 LAB 4

$$R_{TH} = \frac{V_{OC}}{I_{SC}}$$

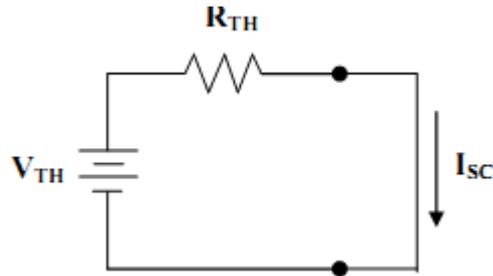


### Apparatus Needed

- Trainer Board (Bread board)
- DC Voltmeter
- DC Ammeter
- Four Rheostats
- One multimeter
- Connecting wires

### Procedure


#### For original circuit

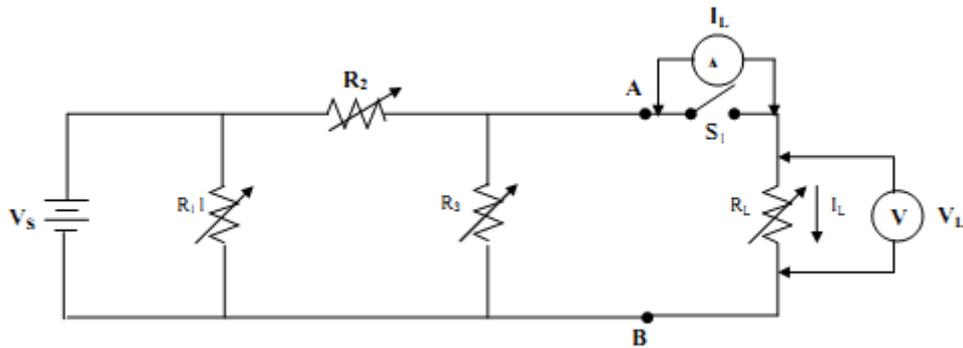1. Arrange the original circuit as shown in the figure below. Apply 5 V dc from power supply. Use suitable fixed resistors for R1, R2 and R3.
2. Measure  $V_L, I_L$  for three values of  $R_L$  & record the data in the table



#### Finding $V_{TH}$ and $R_{TH}$

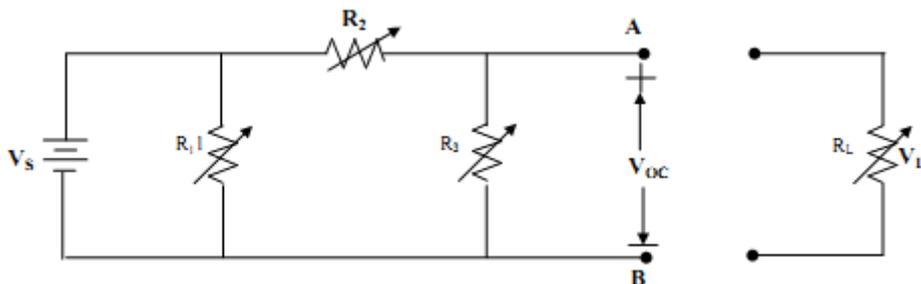
3. Remove the load resistance and find the open circuit voltage between terminals A & B. This voltage is Thevenin Voltage i.e.  $V_{TH} = V_{oc}$



4. Place a short circuit between terminals A & B and find the short circuit current  $I_{SC}$ . Divide the open circuit voltage by the short circuit current to find the Thevenin Resistance  $R_{TH}$  i.e.

$$R_{TH} = \frac{V_{OC}}{I_{SC}}$$


## CSE 122 LAB 4

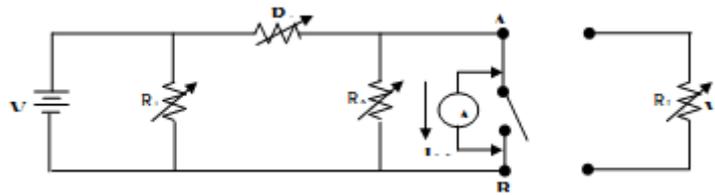

Alternatively find the Thevenin resistance by opening  $R_L$ , disabling the voltage source and measuring the resistance across terminal AB using multimeter and verify that in both cases the resistance is same.
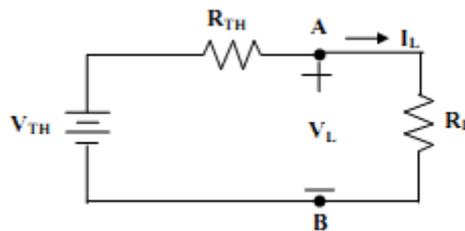
### For Thevenin Equivalent Circuit

- Construct the Thevenin's equivalent circuit as shown in figure below setting the power supply at  $V_{TH}$  volts and the rheostat at  $R_{TH}$  ohms. Now measure the load current  $I_L$  and the load voltage  $V_L$  for the values of  $R_L$  determined in step 2. Compare these values with previous values.



### Tables

**Table1:** Data for Original circuit  $R_1=$  ,  $R_2=$  ,  $R_3=$  ,  $V_S=$

No. of Obs.	Values of $R_L$	Load Voltage $V_L$	Load current $I_L$
1.			
2.			
3.			

$V_{TH} =$  ,  $R_{TH} =$

**Table2:** Data for Thevenin equivalent circuit

No. of Obs	Values of $R_L$	Load Voltage $V_L$	Load current $I_L$
1.			
2.			
3.			

### Result

- Find theoretically the Thevenin equivalent circuit for the values of  $R_0$ ,  $R_2$ ,  $R_3$  &  $V_S$  recorded in table. Also find  $I_L, V_L$ .
- Show the results in tabular form
- Comment on the obtained results and discrepancies